

Instructions:

1. Use Behavioral and Dataflow modelling for this experiment.
2. Perform RTL simulation using the provided testbench and tracefile.
3. Perform Scan-Chain on Xenon Board to verify the functionality
4. Demonstrate the observations to your TA.

Problem Statement

1. Describe the given ALU using VHDL. This ALU circuit performs various functions based on select lines.

 


Figure 1: ALU with 4 functions

S1 S0	ALU Output
0 0	Concatenate two 4-bit inputs A and B
0 1	Performs A-B Operation
1 0	Performs A xor B Operation
1 1	Produces output as 2^*A

- Simulate your design using the generic testbench to confirm the correctness of your description.
- **Tracefile** format $< S1\ S0\ A3\ A2\ A1\ A0\ B3\ B2\ B1\ B0 > < Y7\ Y6\ Y5\ Y4\ Y3\ Y2\ Y1\ Y0 >$ 11111111
- You can use the skeleton code given below:

```

library ieee;
use ieee.std_logic_1164.all;

entity alu_beh is
  port (
    A: in std_logic_vector(3 downto 0);
    B: in std_logic_vector(3 downto 0);
    sel: in std_logic_vector(1 downto 0);
    op: out std_logic_vector(7 downto 0)
  ) ;
end alu_beh;

architecture a1 of alu_beh is

  function sub(A: in std_logic_vector(3 downto 0); B: in std_logic_vector(3 downto 0))
    return std_logic_vector is
    -- declaring and initializing variables using aggregates
    variable diff : std_logic_vector(.....):=(others =>'0');
    variable carry: std_logic_vector(.....):=(others =>'0');
  begin
    -- Hint: Use for loop to calculate value of "diff" and "carry" variable
    -- Use aggregates to assign values to multiple bits
    return diff;
  end sub;

begin
  alu : process( A, B, sel )
  begin
    -- complete VHDL code for various outputs of ALU based on select lines
    -- Hint: use if/else statement
    --
    -- sub function usage :
    --   signal_name <= sub(A,B)
    --   variable_name := sub(A,B)
    --
    -- concatenate operator usage:
    --   "0000" & A
  end process ; --alu
end a1 ; -- a1

```